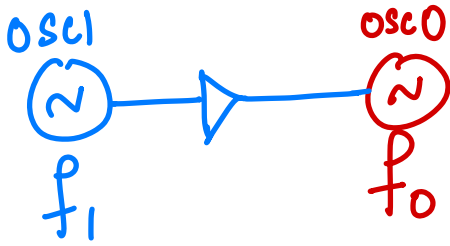




# Injection Locking - Introduction

What is injection locking?



aka  
"Entrainment"

If  $|f_1 - f_0| \leq \Delta f$ ,  
then osc0 spontaneously  
oscillates at  $f_1$  & has  
a well defined phase  
relationship with osc1.

What if  $|f_1 - f_0| > \Delta f$ ?

Then you get Injection Pulling, where  
osc-0 tries to lock but fails  
 $\Rightarrow$  Spectrum gets spread out or "corrupted"

Why do we care?

1) One clean signal (PLL), it can be easily  
duplicated.  $\Rightarrow$  Better phase noise performance  
& freq. stability.

2) Quadrature signal generation.  $90^\circ \rightarrow 0^\circ$



3) Sub-harmonic & Super-harmonic locking.




\* 4) > Large scale phase arrays at MM-wave & for wireless power transfer.

> Ising machines for NP-Hard combinatorial problems.

5) Pulling is generally considered bad!  
(So we want to avoid it)

# Intuition - (From a circuit design perspective)

## Concept #1

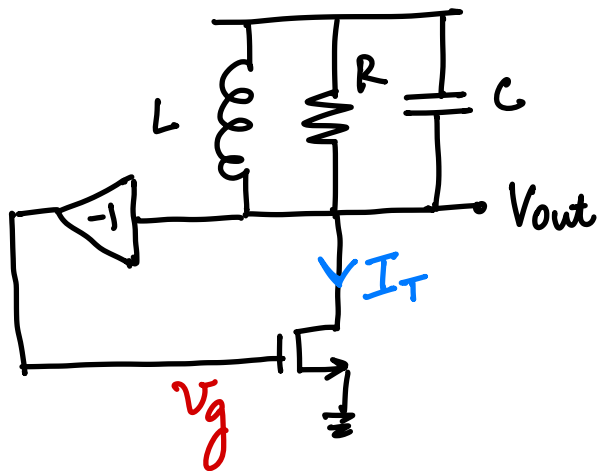

$$\frac{V_{out}}{I_T} = 180^\circ \quad \left| \quad \frac{V_{DD} - V_{out}}{I_T} = R$$


(Assume Barkhausen to be true)

► If the loop gain is 1  $\Rightarrow$  oscillates!





$\Rightarrow$  circuit oscillates at  $\omega_0 \rightarrow$  resonance freq. of the tank  $= \frac{1}{\sqrt{LC}}$


## Concept #2

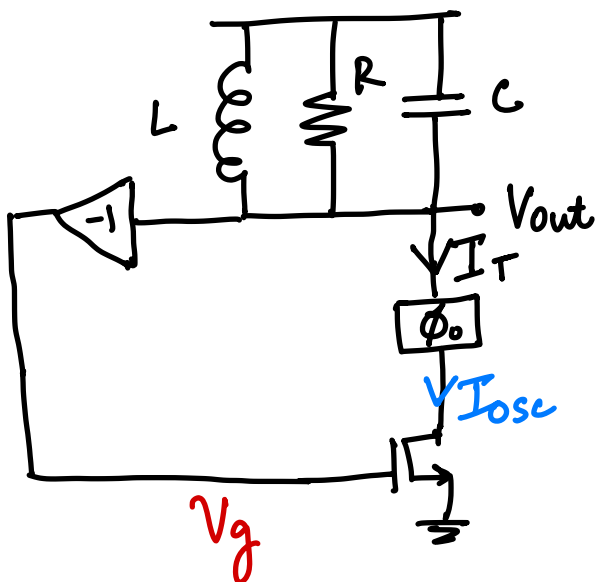

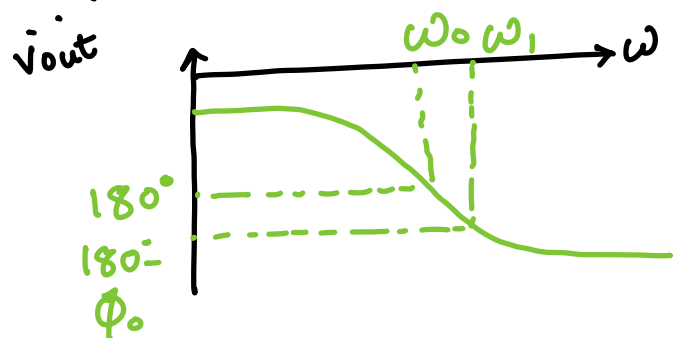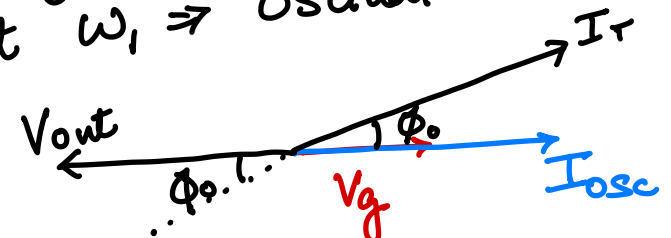"Loop gain condition is satisfied at  $\omega_1 \Rightarrow$  oscillation occurs at  $\omega_1$ ."



# Concept #3

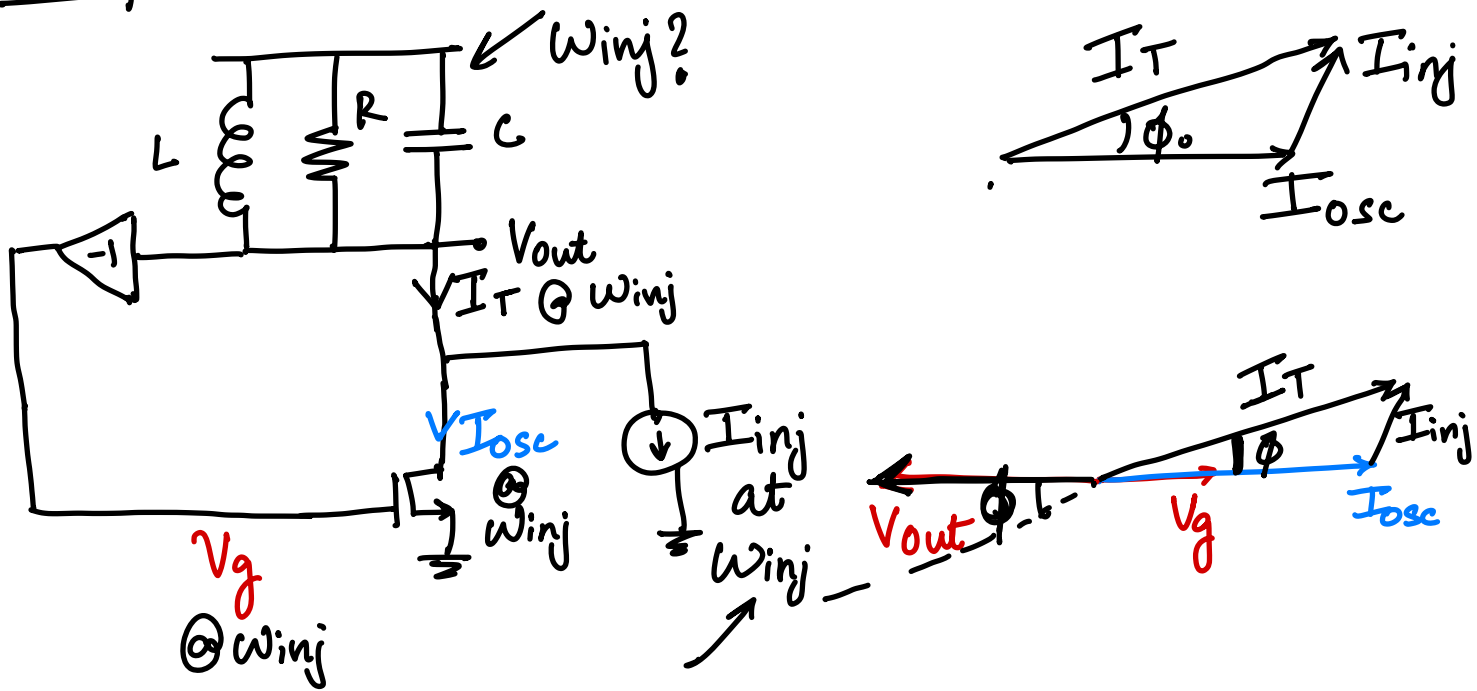


## Mechanism

- >  $\omega_{inj}$  is injected into oscillator
- > At  $\omega_{inj}$ , the tank phase is offset by  $\phi_0$
- > The oscillator "locks" onto  $\omega_{inj}$  with a phase that cancels  $\phi_0$  to restore the loop phase condition at  $\omega_{inj}$ !

" $I_{osc}$  adjusts its phase w.r.t the injection to satisfy loop phase condition at  $\omega_{inj}$ "

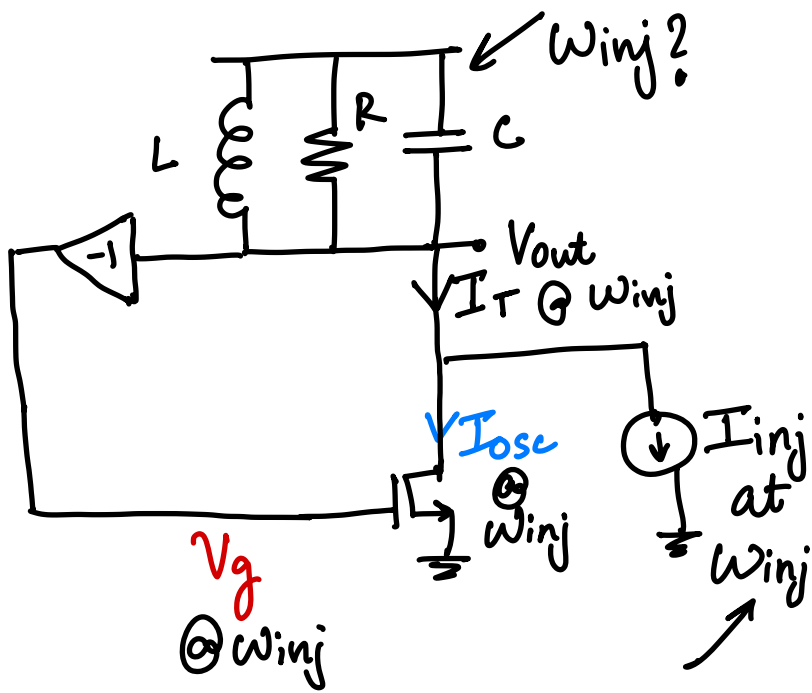$\omega_{inj}$   $\xleftrightarrow[\text{Equation}]{\text{Ader's}}$   $I_{osc}$  phase when locked!



Loop Phase =  $360^\circ$

